

## Logic Design II

CSci 2021: Machine Architecture and Organization  
Lecture #37, April 27th, 2015

Your instructor: Stephen McCamant

1

## Truth Tables

- **Combinational circuit = Boolean function**
  - Combinational: no cycles or memory
  - Outputs are determined just by inputs
- **Finite size**
  - A Boolean function has a finite representation
  - If  $i$  input bits,  $2^i$  possible input combinations
  - Can study by just writing the output for all possible inputs
- **Truth table**
  - Standard way to write a function
  - $2^i$  rows, input combinations in increasing order
  - One column per intermediate or output

2

## Truth Table Example

a	b	c	(a & b)	(a & b)   c
0	0	0	0	0
0	0	1	0	1
0	1	0	0	0
0	1	1	0	1
1	0	0	0	0
1	0	1	0	1
1	1	0	1	1
1	1	1	1	1

3

## Equivalences with a Truth Table

- **Check whether two Boolean formulas are equal**
  - Write truth table covering both
  - Check two columns have all the same entries
- **Advantages**
  - Straightforward
  - No algebraic insight needed
- **Disadvantages**
  - Effort exponential in number of input bits

4

## Equivalence Example

a	b	c	(b & c)	a   (b & c)	(a   b)	(a   c)	(a   b) & (a   c)
0	0	0	0	0	0	0	0
0	0	1	0	0	0	1	0
0	1	0	0	0	1	0	0
0	1	1	1	1	1	1	1
1	0	0	0	1	1	1	1
1	0	1	0	1	1	1	1
1	1	0	0	1	1	1	1
1	1	1	1	1	1	1	1

5

## Combinational Logic Design

- **Given: description of circuit behavior**
  - Word problem, or truth table
- **Goal: efficient circuit implementation**
  - Usually most important: fewest gates and wires
  - Secondly: reduce number of levels (propagation delay)
- **Kinds of techniques**
  - Up to 6 inputs: pencil and paper approaches
  - Large but structured: split into repeated pieces
  - Large and unstructured: computer algorithm

6

## DNF / SOP

- An input or its negation is called a *literal*
  - E.g.: a, !b
- An AND of literals is a *product term* or *cube*
  - E.g.: (a & c), (a & !b), (!a & !b & !c), c
- An OR of product terms is a *sum of products (SOP)*, or in *disjunctive normal form (DNF)*
  - E.g.: (a & b) | (a & c)
- (Dual: *product of sums (POS)*, or *conjunctive normal form (CNF)*)

7

## Truth Table → SOP

- Simple but not very efficient
- Create a product term for each 1 entry
- Example with XOR:

a	b	a ^ b
0	0	0
0	1	1
1	0	1
1	1	0

Result: (a & !b) | (!a & b)

- (Also possible: dual with 0s and CNF)

8

## Inefficiency of Straight DNF

- Consider another example:

a	b	b
0	0	0
0	1	1
1	0	0
1	1	1

Result: (!a & b) | (a & b)

- By algebra, can simplify back to “b”
  - Factor, (!a | a) = 1, 1 & b = b
- Can we recognize these patterns earlier?

9

## Logistics Intermission

- Sorry, no quiz 2s today
  - Good chance of grades by tomorrow and papers Wednesday
- Cache Lab due tonight
  - Moodle has been having some slowness
  - Suggest you allow a little extra time for final submission
- Assignment V out on Wednesday
  - Mostly logic design


10

## Karnaugh Map Idea

- Write truth table entries in an array
- Product terms represented by certain rectangles
- Visually, find small number of rectangles to cover 1 bits
  - OK to cover more than once, combine with OR
  - Fewer rectangles = smaller circuit

11

## 2-variable “Karnaugh Map”

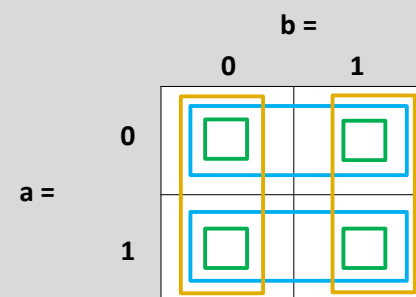

12

## 2-variable "Karnaugh Map" example

**Result:**  
 **$\neg a \mid b$**

		b =	
		0	1
a =	0	1	1
	1	0	1

13

## Extending to 3 and 4 Variables

- Put two variables on a side
  - Weird order: 00 01 11 10
  - "Gray Code": change only one bit at a time
- Rectangles can enclose 1, 2, 4, or 8 entries
  - Bigger is better
- Rectangles can wrap around the edges
  - 00 is adjacent to 10

14

## 4-variable Karnaugh Map Example

		ab =				
		00	10	11	01	
cd =	00	0	1	0	1	(a & !b)
	10	0	1	0	0	(a & d)
	11	0	1	1	0	(!a & b & !c & !d)
	01	0	1	1	0	


15

## Extending to 5 and 6 Variables

- 2D is no longer enough
  - No way to order 3 variables to capture 12 adjacencies
- Approach: stacking
  - Make 2 (for 5 inputs) or 4 (for 6 inputs) 4-input Karnaugh maps
  - Corresponding entries are "on top of" each other
  - Rectangles become 3D
  - Usually still drawn as 2D
  - With 6, more possibilities for wrapping too

16

## 5-variable Karnaugh Map Example

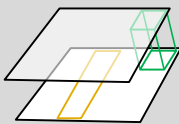

0	1	0	1
0	1	0	0
0	1	1	0
0	1	1	0

0	0	0	1
0	0	0	0
0	1	1	0
0	1	1	0

17

## Karnaugh Map Tips: Overlap is Good

		ab =			
		00	10	11	01
cd =	00	0	1	0	0
	10	0	1	0	0
	11	0	1	1	0
	01	0	1	1	0

18

### Karnaugh Map Tips: No 3s

		ab =			
		00	10	11	01
cd =	00	0	0	0	0
	10	0	1	0	0
	11	0	1	0	0
	01	0	1	0	0

19

### Karnaugh Map Tips: Wrap Around

		ab =			
		00	10	11	01
cd =	00	1	0	0	1
	10	0	0	0	0
	11	0	0	0	0
	01	1	0	0	1

!a & !c

20

### Don't Cares

- Some results don't matter
  - Domain of function is a subset of all n-bit strings
  - Unused bit patterns in encodings
  - Bits sometimes ignored by other circuits
- "Don't care" value could be 0 or 1
  - Usually denoted by X
- Don't-cares allow designs to be simpler
  - Choose the value that allows a simpler circuit
- In early CPUs, led to undocumented instructions
  - Example: x86 ASL vs. SHL
  - On modern CPUs, more error checking

21

### Karnaugh Map Tips: Don't Cares

		ab =			
		00	10	11	01
cd =	00	X	0	X	1
	10	0	X	X	X
	11	X	X	X	X
	01	1	X	X	X

22

### Dual (POS) Karnaugh Maps

		ab =			
		00	10	11	01
cd =	00	1	1	1	1
	10	1	1	0	1
	11	1	1	0	1
	01	1	1	1	1

- Pretend 0s are 1s
  - And vice-versa
- Negate final result

!(a & b & c)

!a | !b | !c

23

### Karnaugh Map: Try Yourself

		ab =			
		00	10	11	01
cd =	00	1	0	0	0
	10	1	1	0	0
	11	1	1	1	1
	01	1	1	0	1

24

## Automated Methods

- **Karnaugh maps don't scale well beyond 6 inputs**
- **Good job for a computer!**
- **Quine-McCluskey algorithm**
  - Tabular analog to Karnaugh maps
  - Optimal, but suffers from exponential blowup
- **Heuristic methods like "espresso"**
  - First, greedily achieve coverage
  - Then, opportunistically improve
  - No optimality guarantee, but good scalability
- **Now a standard part of CAD systems**
  - Like compilers for software

25