

Logic Design IV

CSci 2021: Machine Architecture and Organization
Lecture #39, May 1st, 2015

Your instructor: Stephen McCamant


1

Sequential Circuits

- Introduce elements that keep state
- Cyclic connections between gates
- Makes more interesting computations possible
 - Processing changing inputs over time
 - E.g., CPU
- Raises more issues related to timing
 - Coordinating timing of operations
 - Time margins for reliable operation
 - Avoiding transient incorrect results

2


Paired Inverters

 

- Good: maintains a particular state
- Bad: no way to set

3

S-R Latch

 

4


Coordination and Clock Signals

- In sequential design, must control when events occur
- Standard approach: clock signal
 - Alternates between 0 and 1
 - Same signal used throughout circuit
 - Challenge in high-speed designs: propagation speed
 - Rate controls speed of entire circuit
 - Design circuit to allow highest possible clock speed
 - Example: 3.0 GHz CPU
- Use clock to control when sequential devices “read”

5

Level-sensitivity

 - First approach:
 - Value updated only when an enable signal (E) is high
 - Called a “level-sensitive” or “gated” device
- Example: gated S-R latch



- Implementation: AND E with S and R inputs

6

Transparency

- **Definition:**
 - A device is transparent if input changes immediately propagate to the output
 - S-R latch is an example
- **Transparent devices in series**
 - Connect output of one latch to input of another
 - Input causes both devices to change at the same time
 - Undesirable in many situations
 - E.g., remember Y86 pipeline stages


7

Edge-triggered Devices

- **Idea: update only on a clock "edge":**
 - Positive/rising edge: 0 to 1
 - Negative/falling edge: 1 to 0
 - One update per clock cycle
- **An edge-triggered bit-storage device is a "flip-flop"**
- **Flip-flops in series:**
 - Previous output changes only after next input is "read"
 - Leads to lock-step propagation, one flip-flop per cycle

8


D Flip-Flop

 

- **Triangle indicates clock input**
 - No bubble → rising edge triggered
- **On edge, store the value of D ("data")**
- **This was our main building block for Y86 registers**
- **!Q is often unused, but available for free**

9


S-R to D

 

- **D = 1: S = 1, R = 0**
- **D = 0: S = 0, R = 1**
- **Avoids ever having S and R together**
- **Trickier: how to build edge-triggering?**

10


Transient Timing

 

- **What does this circuit do?**
- **Functional perspective:**
 - $(x \& !!x) = (x \& !x) = 0$, useless?
- **Actually, rising edge of x causes a brief output pulse**
 - Fast path goes to 1 before delayed path goes to 0

11


Master-slave D Flip-Flop

 

- **Make flip-flop out of two gated latches**
- **Updates only on rising clock edge**
 - Master freezes first
 - Then slave is enabled

12


T Flip-Flop

 

- Another input style, T = “toggle”
- Flip-flop behavior summarized by state update formula
 - Here, $Q' = (Q \wedge T)$
 - T = 0: unchanged; T = 1: value is negated
- Would this make sense without a clock?

13

J-K Flip-Flop

 

- More powerful input type
 - Like combination of S-R and T
- Cases:
 - J = K = 0: no change
 - J = 1; set; K = 1: reset
 - J = K = 1: toggle
- $Q' = (Q \& !K) \mid (!Q \& J)$

14

Propagation Delay and the Clock

- Combinational circuits take time
 - Most important: gate input to gate output propagation
 - Less significant: signal propagation on wires
- Worst-case circuit timing
 - Conceptually, consider all input to output paths
 - For each path, sum maximum component times
 - Worst case depends on slowest path
- Timing determines maximum clock speed
 - Consider slowest flip-flop to flip-flop path
 - Too-fast clock causes incorrect results


15

Hazards and Glitches

- Glitch:
 - A transient circuit output that differs from the ideal output
- (Logic) hazard:
 - Circuit feature that makes glitches possible
- When?
 - Unexpected values appear while changes are propagating
- Easiest option:
 - Use clocks and flip-flops (registers) so that circuit outputs matter only after they have settled
- Sometimes needed:
 - Redesign circuit or add gates to prevent hazards

16

Logic Hazard Example

 

- Static-1 hazard:
 - (a, b, c) = (1, 1, 1) and (0, 1, 1) should both output 1
 - Depending on delay, a 0 glitch may occur

17


Timing for Flip-Flops

- Input must be steady around clock edge for reliable operation
 - Setup time: amount of time before clock input must be right
 - Hold time: amount of time after clock that input must right
- Delay before output changes
 - Clock-to-output time: delay between clock edge and output edge
- Important fact:
 - (hold time) < (clock-to-output time)
 - If true of two flip-flops, it is safe to connect output of one to input of another, on the same clock

18

Metastability


- **Analogy:**

 

- **Flip-flop tries to return to a stable state**
 - Self-correcting feedback
- **But, if close to metastable point:**
 - Might take a long time to “decide”
 - Must avoid this situation for a reliable circuit

19

Shift Register

 

- **Flip-flops connected in series**
- **Behavior:**
 - Sequence of bits each move one stage per clock cycle
- **Variations:**
 - Serial or parallel input
 - Series or parallel output
 - Shift only one some cycles

20

Counters

- **Simple kind of time-varying digital system**
 - Produces a single sequence of states, repeating
 - Changes every cycle or on a count pulse
- **Example: 3-bit binary up-counter**
 - Produces 000, 001, 010, 011, 100, 101, 110, 111, 000, 001, ...
- **Variations:**
 - Down-counters
 - Decade counters (for decimal): 0 through 9
 - Gray code: sequence where only one bit changes at a time
 - Ring counter: circular shift register producing one-hot outputs

21


State Machines

- **State machine perspective:**
 - If a device has limited memory, we can enumerate its possible *states*
 - n bits of memory \rightarrow at most 2^n states
 - Inputs cause state transitions
 - Outputs depend on state and possibly inputs
- **General approach for designing sequential circuits**
 - Enumerate states
 - Determine state transitions and I/O
 - Last two summarized in *state transition diagram*
 - Use flip-flops to remember state
 - Use combinational logic to implement update and output functions

22

Counters as State Machines

 - **Simplified special case**
 - Output is generally identical to state
 - No input other than a clock
 - State transition diagram is a single cycle
- **Three-bit up counter:**



23